

# TECHNICAL PAPER

## Transducer electrical equivalent circuit

### Traditional model

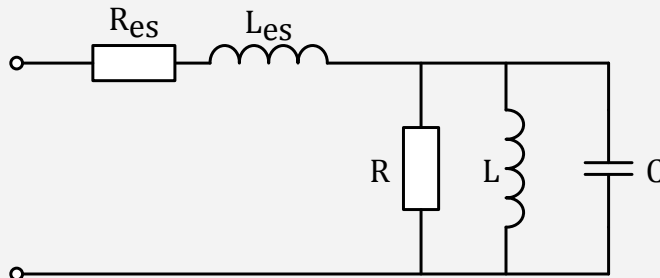


Fig. 1

$$L = (Bl)^2 \times C_{ms}$$

$$C = \frac{M_{ms}}{(Bl)^2}$$

$$R = \frac{(Bl)^2}{R_{ms}}$$

$M_{ms}$	Driver moving mass incl. air
$C_{ms}$	Driver suspension compliance
$R_{ms}$	Driver mechanical loss
$Bl$	Driver force factor
$R_{es}$	Voice coil DC resistance
$L_{es}$	Voice coil inductance

This page shows the differences between the traditional loudspeaker model (fig. 1 above) and the Wright empirical model (fig. 2 below).

The only difference between the two models is that the inductor  $L_{es}$  of the traditional model has been replaced by a more complicated component with frequency dependent

$$Z_{em} = K_{rm} \times \omega^{E_{rm}} + j \times K_{xm} \times \omega^{E_{xm}} \quad \omega = 2\pi f$$

While the traditional model in many cases is very inaccurate at higher frequencies, the Wright model is usually much more accurate. There is not a big difference at low frequencies (bass tuning, for instance) but for crossover designs the traditional model is often not usable.

### Wright empirical model

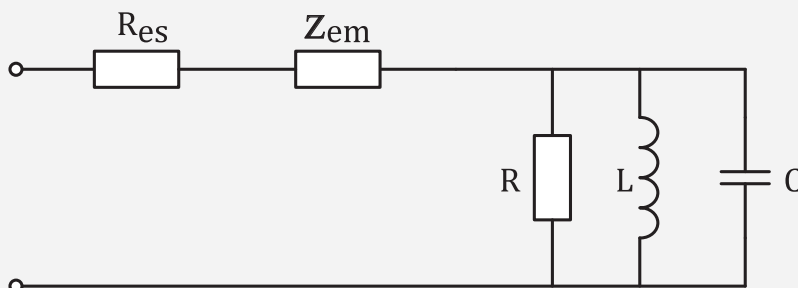


Fig. 2

$$L = (Bl)^2 \times C_{ms}$$

$$C = \frac{M_{ms}}{(Bl)^2}$$

$$R = \frac{(Bl)^2}{R_{ms}}$$

$M_{ms}$	Driver moving mass incl. air
$C_{ms}$	Driver suspension compliance
$R_{ms}$	Driver mechanical loss
$Bl$	Driver force factor
$S_D$	Driver effective cone area
$R_{es}$	Voice coil DC resistance
$Z_{em}$	Replaces $L_{es}$ from the traditional model

REFERENCES. J. R. Wright, "An empirical model for loudspeaker motor impedance", J. Audio Eng. Soc., Vol. 38, No. 10, 1990.