

TECHNICAL PAPER

Transducer electrical equivalent circuit

Traditional model

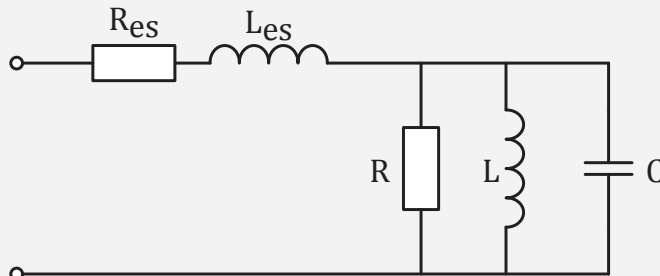


Fig. 1

$$L = (Bl)^2 \times C_{ms}$$

$$C = \frac{M_{ms} \times S_D^2}{(Bl)^2}$$

$$R = \frac{(Bl)^2}{R_{ms}}$$

M_{ms}	Driver moving mass incl. air
C_{ms}	Driver suspension compliance
R_{ms}	Driver mechanical loss
Bl	Driver force factor
S_D	Driver effective cone area
R_{es}	Voice coil DC resistance
L_{es}	Voice coil inductance

This page shows the differences between the traditional loudspeaker model (fig. 1 above) and the Wright empirical model (fig. 2 below).

The only difference between the two models is that the inductor L_e of the traditional model has been replaced by the two components R_{em} and L_{em} in the Wright model. R_{em} is a resistor and L_{em} is an inductor but both components are frequency (f) dependent:

$$R_{em} = K_{rm} \times (2 \times \pi \times f)^{E_{rm}}$$

$$L_{em} = K_{xm} \times (2 \times \pi \times f)^{[E_{xm}-1]}$$

While the traditional model in many cases is very inaccurate at higher frequencies, the Wright model is much more accurate. There is not a big difference at low frequencies (bass tuning, for instance) but for crossover designs the traditional model is often not usable.

Wright empirical model

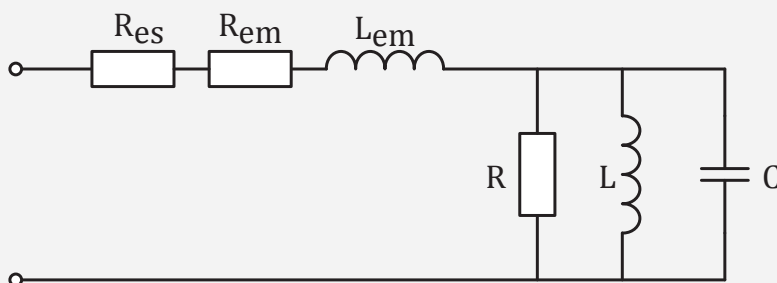


Fig. 2

$$L = (Bl)^2 \times C_{ms}$$

$$C = \frac{M_{ms} \times S_D^2}{(Bl)^2}$$

$$R = \frac{(Bl)^2}{R_{ms}}$$

M_{ms}	Driver moving mass incl. air
C_{ms}	Driver suspension compliance
R_{ms}	Driver mechanical loss
Bl	Driver force factor
S_D	Driver effective cone area
R_{es}	Voice coil DC resistance
R_{em} and L_{em}	Replace L_{es} from the traditional model

REFERENCES. J. R. Wright, "An empirical model for loudspeaker motor impedance", J. Audio Eng. Soc., Vol. 38, No. 10, 1990.